



$$i_{R_1} = \frac{V_- - V_0}{R_1}, \quad i_C = C \frac{d}{dt} (V_- - V_0) = \frac{V_0}{R_2}$$

From  $i_L = i_C + i_{R_1}$

$$i_L = \frac{V_0}{R_2} + \frac{V_- - V_0}{R_1} \Rightarrow V_0 = \frac{R_2 (i_L R_1 - V_-)}{R_1 - R_2}$$

Plug  $V_0 = \dots$  in  $C \frac{d}{dt} (V_- - V_0) = \frac{V_0}{R_2}$

$$C \frac{d}{dt} \left( V_- - \frac{R_2}{R_1 - R_2} (i_L R_1 - V_-) \right) = \frac{1}{R_2} \frac{R_2 (i_L R_1 - V_-)}{R_1 - R_2}$$

$$C R_1 \frac{d}{dt} V_- + V_- = C R_1 R_2 \frac{d i_L}{dt} + R_1 i_L$$

$$V_- = \underbrace{C R_1 R_2 \frac{d i_L}{dt}}_{\text{Simulated inductance.}} + \underbrace{R_1 i_L}_{\text{resistance of the inductor}} - \underbrace{C R_1 \frac{d}{dt} V_-}_{\text{small correction}} \approx \text{neglect.}$$